



**Associazione Radioamatori Italiani \* Sezione di Cassano delle Murge (Bari) – Italy**

*\* A.R.I. Member Club Founded on June 5th 2004 \**

***“Amicizia Attraverso la Radio \* Friendship Through Radio”***

*A.R.I. Associazione Radioamatori Italiani previously Associazione Radiotecnica Italiana (1927 – 1977)*

***IQRP#669 \*Club Call-sign: IQ7MU \* G-QRP#11827***

*President: Giancarlo MODA, I7SWX*

## **EXTENDING SOFTROCK40 OTHER QSD AND TAYLOE DETECTOR TO HF MULTIBAND COVERAGE**

**Giancarlo MODA, I7SWX**

During our Radioclub General Annual Meeting, on June 18th 2005, a presentation on Software Defined Radio and in particular about the SoftRock40 kits was arranged. Club members and also visitors from some local radio clubs were very taken by this new technology. A decision was taken, as part of the Club activities, to help members and other Italian Radio Amateurs to get hold of the SoftRock kits. An agreement was arranged with Tony Parks, KB9YIG, to help our Club to manage the purchase and shipments of kits to Italy for those homebrewers not able to do it directly.

Normally people start eating chocolate formed with low cacao and high milk percentages moving to higher cacao and lower milk mixture till nearly 100% cacao and no milk. My feeling is that something similar has happen and is happening to hams that have discovered SDR technology and in particular to those that have purchase Tony's SoftRock40 monoband kits.... Now we want more flavors ... we want to cover with these kits as many ham bands as possible. In theory it is quite easy to do it in real life it may not be so. Key point of an SDR solution is to get image rejection as high as possible but we do have to accept what components limits permits. The highest possible rejection is obtained if our detector or mixer has the output signals I and Q in the highest quadrature possible and also they amplitude must be 100% equal. In real life we are “forced to accept” an hardware image rejection that may be in the range of -25 to -30 dB. Those funny friends of ours that fiddle with software can help us to increase such image attenuation up to around -60 to -70 dB... not on the entire band but at the frequency of interest image. In the future we should be able to have better performances on this aspect. Our quadrature (90 degrees I and Q phases difference) is first produced by our QSD Local Oscillator quadrature signal. To help on the quadrature a Digital Quadrature Generator with a division by four counter is used. If we do need to cover from 1.7 MHz to 30 MHz we will need a variable oscillator generating a signal from below 7MHz to 120MHz. This is not an easy task with available oscillators. Now DDS, using AD9951 chip, may help to solve the problem as they can generate a signal up to around 200MHz, a limit that can help, eventually, to cover the 50MHz band too. We maybe able to fix the local oscillator but we may discover that our counter and QSD chips have something inside that does not permit to have real quadrature output and same amplitude signals. Faster and more performing chips are showing up but not always in a size manageable for a homebrewer.... These aspects force us to compromise as much as possible but, at the same time, trying to get as many benefits as possible too.

Recently I was able to implement and experiment one of my old projects I started on paper at beginning of 2003. The project has been adapted to the SoftRock40 Version 6 and it is the multiband Digital Quadrature Generator circuit diagram reported in Figure 1. This DQG maybe used also for other SoftRock kits like V7 and V5, other SDR like the SDRZero, FireFly, NorCal 2030 and the like.

## CIRCUIT DESCRIPTION

Looking at the circuit diagram in Figure 1, we have on the left the Squarer using two XOR gates. This is followed by other two XOR gates forming the Splitter with two complementary LO signals ( $0^\circ$  and  $180^\circ$ ). The complementary LO signals are feeding the two flip-flops forming the real Digital Quadrature Generator in a configuration to divide by 2 the oscillator signal frequency, delivering 4 phases oscillator signal at fundamental frequency. Phases  $0^\circ$  and  $90^\circ$  form the quadrature LO signal necessary to drive the MUX FST3254 forming the SDR QSD or Tayloe Detector. Phases  $180^\circ$  and  $270^\circ$  are used when the I-Q mixer or QSD are formed by a Fast Bus Switch FST3125. For QSD or Tayloe Detector using the FST3125 a decoder formed by four NAND gates 74ACT00 has to be inserted between the DQG and the switches; such a circuit is reported in Figure 1 on the bottom right. If the FST3126 is used, the decoder requires AND gates 74ACT08.

An external control, employing a multiturns potentiometer, operating as a manual phases or quadrature balance is associated with the Squarer.

## HARDWARE MODS TO IMPLEMENT

Modification should be applied in a non destructive form as to report the assembly to the original conditions.

- 1) Disconnect pins 2 (S1) [ $90^\circ$ ] and 14 (S0) [ $0^\circ$ ] of FST3253 from the PCB tracks. Be careful not to break these pins. Pins 2 and 14 will then be connected to the DQG as in circuit diagram ( $90^\circ$  and  $0^\circ$ )
- 2) In the SoftRock kits replace the simple Band Pass Filter with a more suitable set of BPF for each band or octaves group.
- 3) Replace the input transformer T1 with a more suitable wide band transformer for full HF coverage.
- 4) Solder a wire to form a short circuit across the crystal in the oscillator. This will stop interferences.

## WINDING A BALUN CORE TRANSFORMER

To implement full HF coverage it is necessary to replace the resonant transformer with a wide band transmission line transformer. This transformer is wound on a balun core type #43-2402 or #43-202. For the SR V6 do 3 windings of 4 turns each, while for SR V7 do 5 windings of 4 turns each. Use any enameled wire size that will permit the windings. Pay attention to the secondary windings phase. Drawing and picture should help.

## GAIN REDUCTION

I have also implemented a drastic gain reduction on the SoftRock V6 to reduce ADC saturation. I have added a 1.2kohm resistor in parallel to each 49.9K feedback resistors on the OPAs.

## HOW TO ADJUST IMAGE REJECTION

Once the SoftRock and any other SDR QSD Receiver becomes a multiband RX we have the necessity to tune to a strong signal on each band and look at its image while adjusting the multiturns potentiometer for the maximum image attenuation. Any type of marker should be valid.

To have an idea of how the regulation works and what is happening I have taken some screen shots on some bands using two tones signals. The adjustment is done as to have one of the two tones reduced as much as possible.

Then I have activated the software reduction functionality of Winrad on the 14MHz shots to increase image rejection.

## BANDPASS FILTERS

Band Pass Filters should be implemented for each band and as required. SoftRock V6 input impedance is around 50 ohm with some reactance changing as bands are changed.

## FINAL

I hope you will enjoy this modification to move your single SDR RX to HF multiband. Please keep on mind that as second as the 74AC86 manufacturer the maximum frequency limit is around 60 MHz and due to delay problems with Q and Not Q signals one of the 74AC-ACT74 flip flop may not have the right data input signal to switch at around 60MHz clock.

To facilitate looking at various SDQ QSDs I have added some circuit diagrams.

73

Giancarlo "Gian" MODA

I7SWX

F5VGU

W1-I7SWX

CE-I7SWX

Swl: I1-10089

Member of: ARI 1959; RSGB 1965; I QRP #571; G-QRP #10241; JARL QRP Club #773

President of A.R.I. Sezione di Cassano delle Murge BA #70.10

G-QRP Club Representative for Italy



[www.qsl.net/i7swx](http://www.qsl.net/i7swx)

[i7swx@yahoo.com](mailto:i7swx@yahoo.com)

*Copyright 2007 by Giancarlo Moda, I7SWX*


*Articles expected to be published in English and Italian*

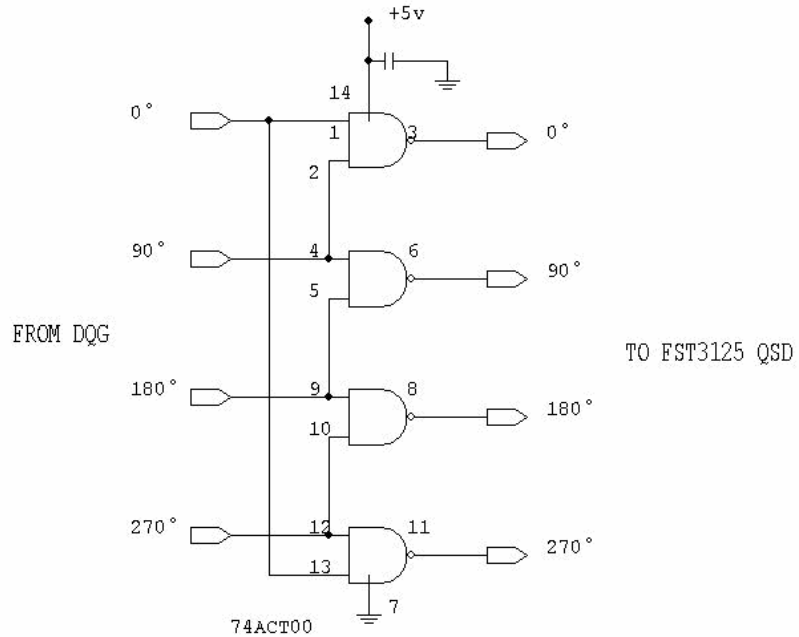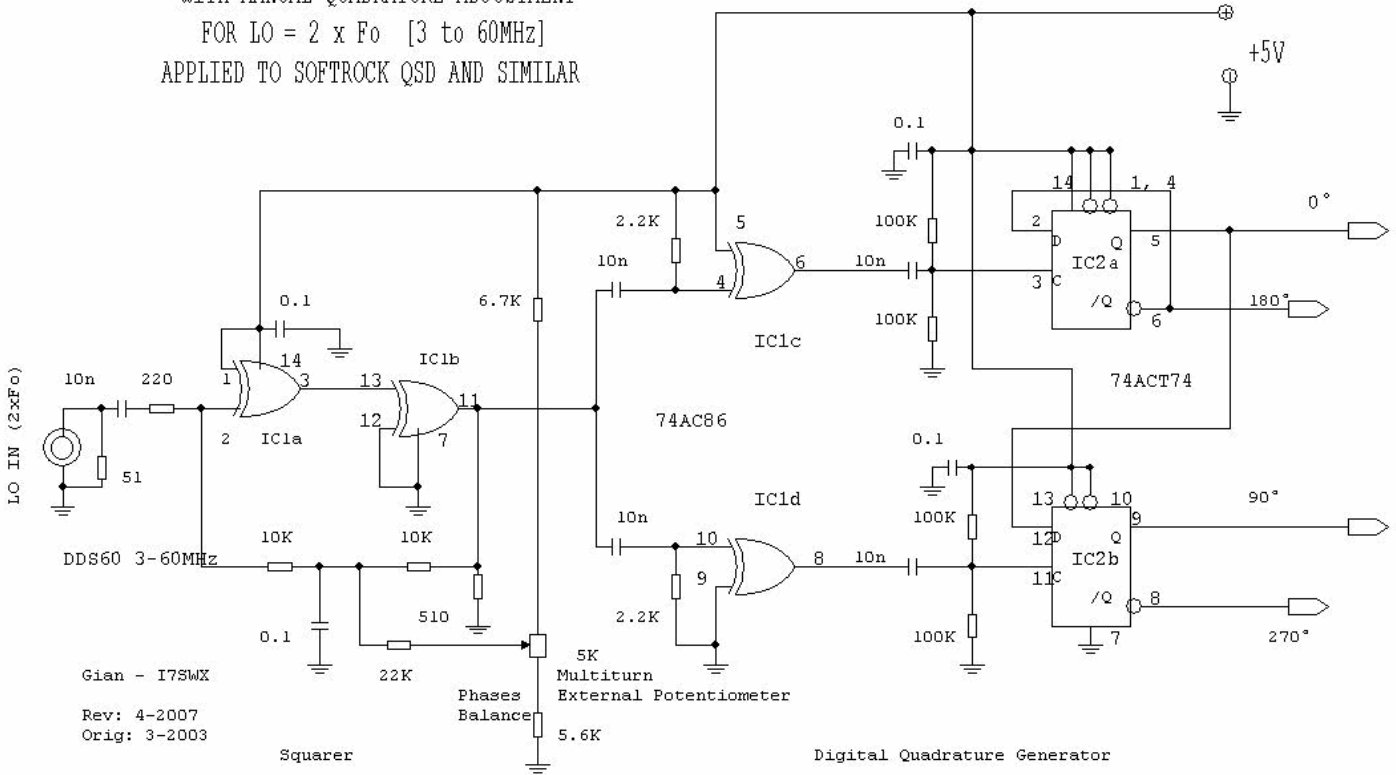I7SWX HF MULTIBAND 1.5 to 30MHz  
 DIGITAL QUADRATURE GENERATOR  
 WITH MANUAL QUADRATURE ADJUSTMENT  
 FOR LO = 2 x Fo [3 to 60MHz]  
 APPLIED TO SOFTROCK QSD AND SIMILAR



Decoder to drive FST3125 switches in QSD and Tayloe Detector applications.  
 When FST3126 are used the NAND 74ACT00 should be replaced by the AND 74ACT08.

# BALUN CORE TRANSFORMER WINDING

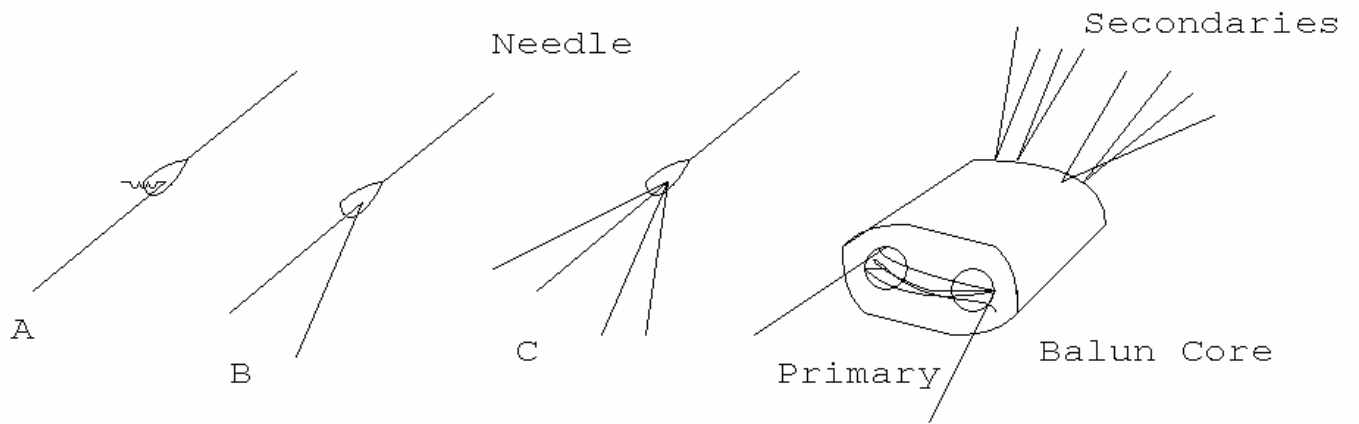


A = 1 Primary winding


B = 2 Secondary windings

C = 4 Secondary windings


Gian, I7SWX

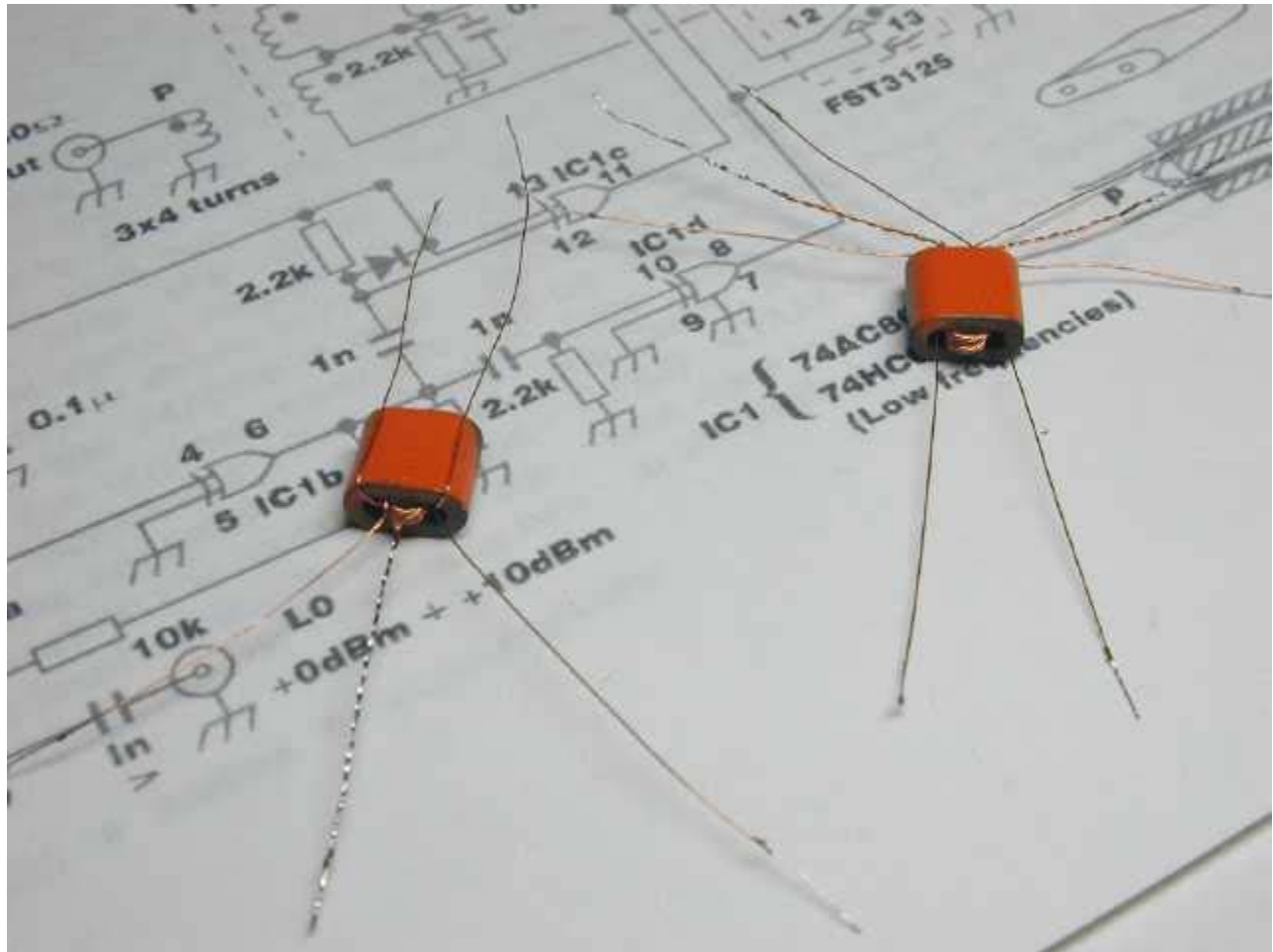

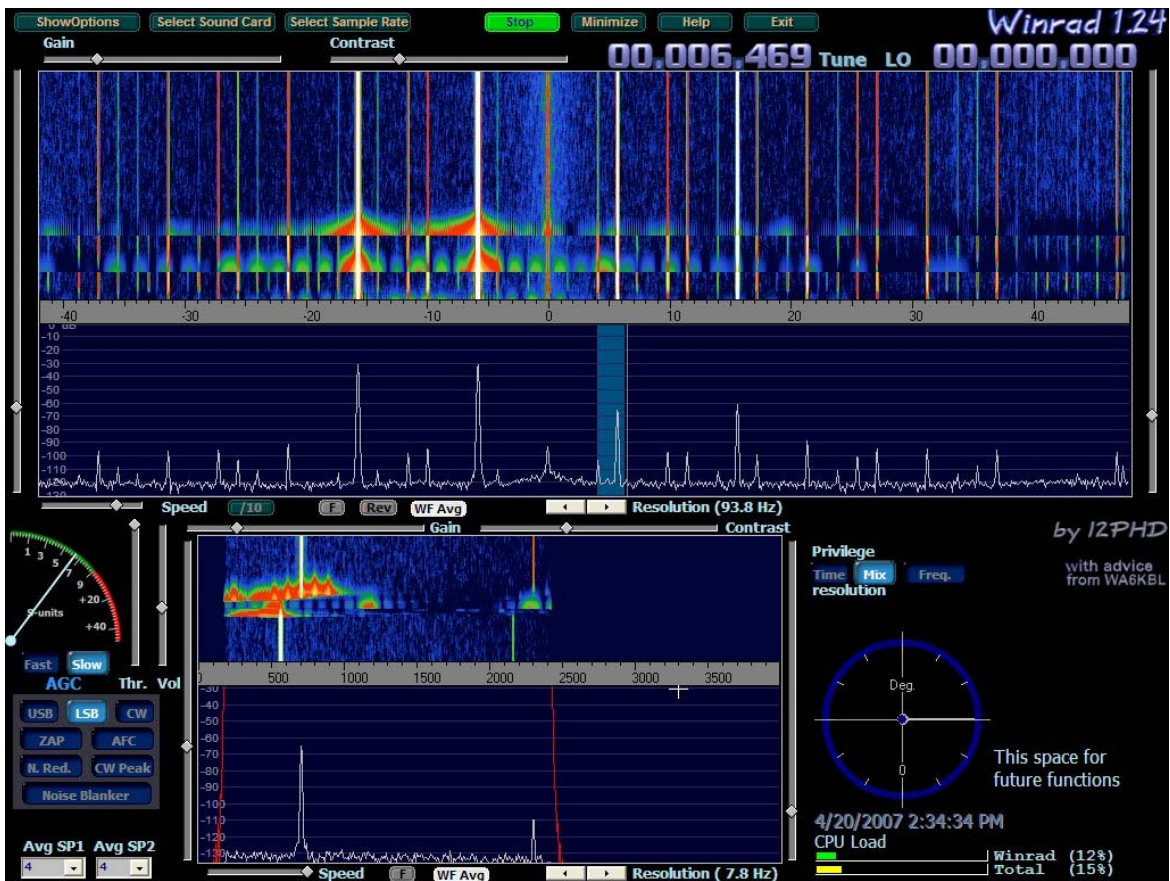
Drawing is illustrating how to wind balun transformers, while the picture should give an idea of the final products



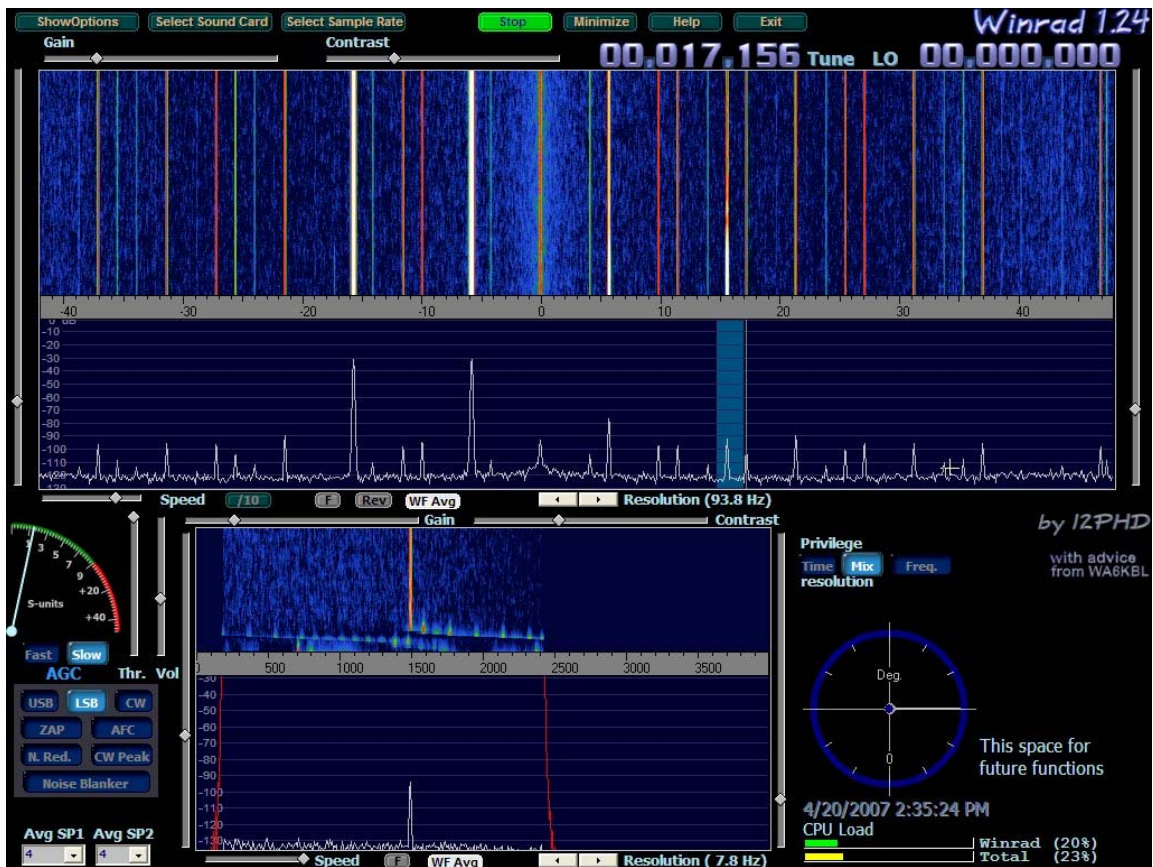
3.5MHz Two Tones before manual hardware adjustment @ -10dBm input



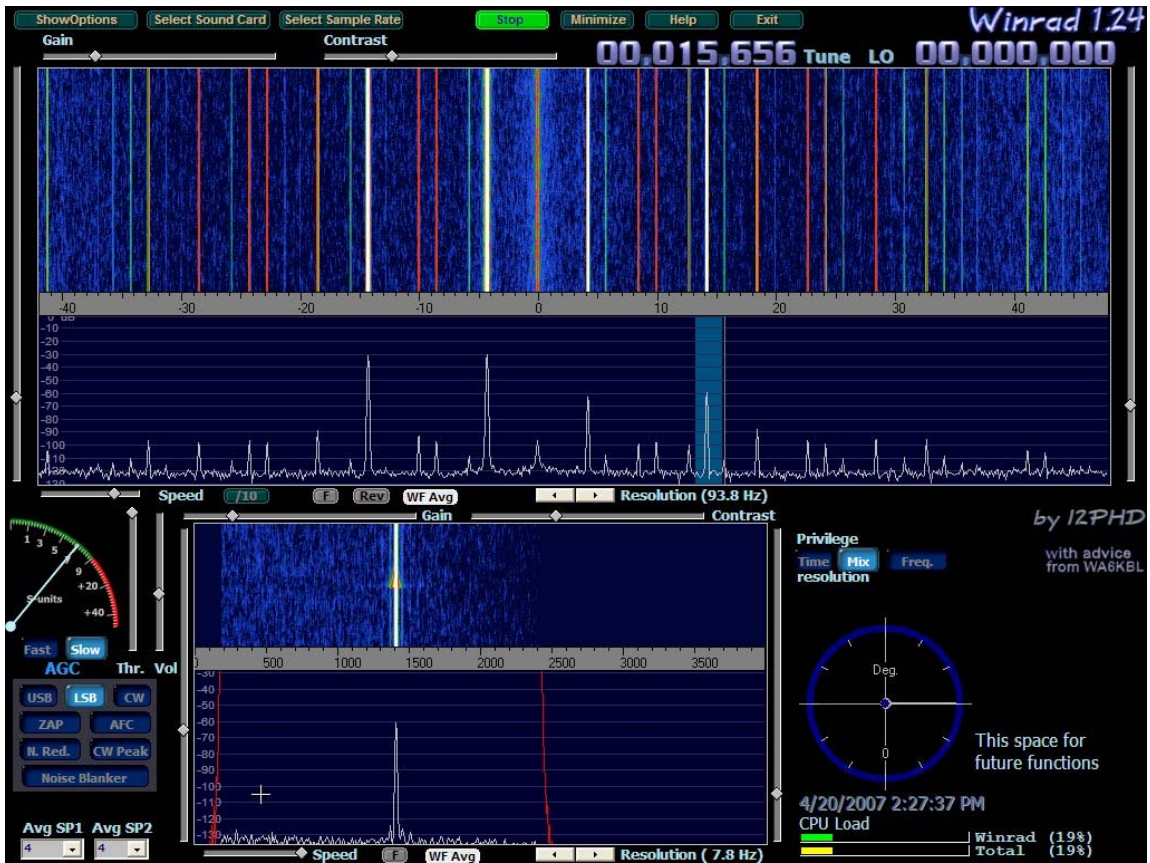
3.5MHz Two Tones after manual hardware adjustment



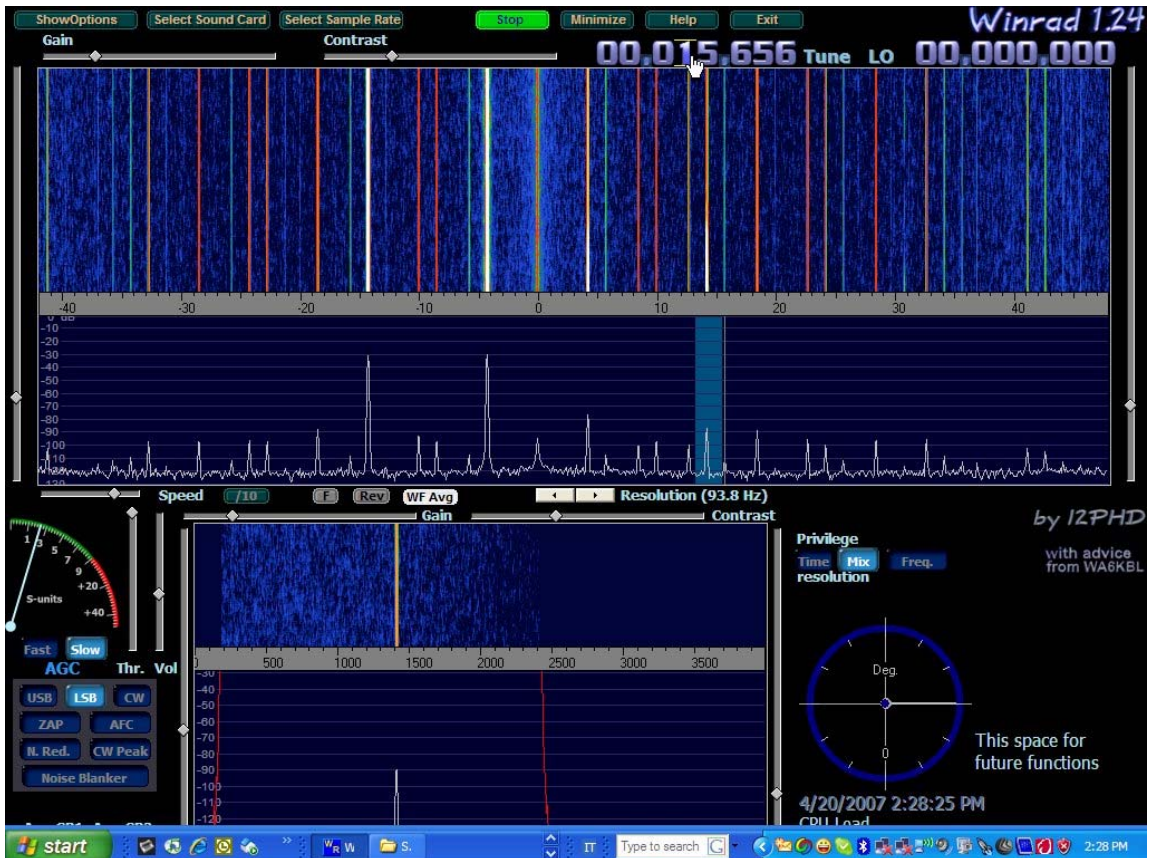
7MHz Two Tones before manual hardware adjustment @ -10dBm



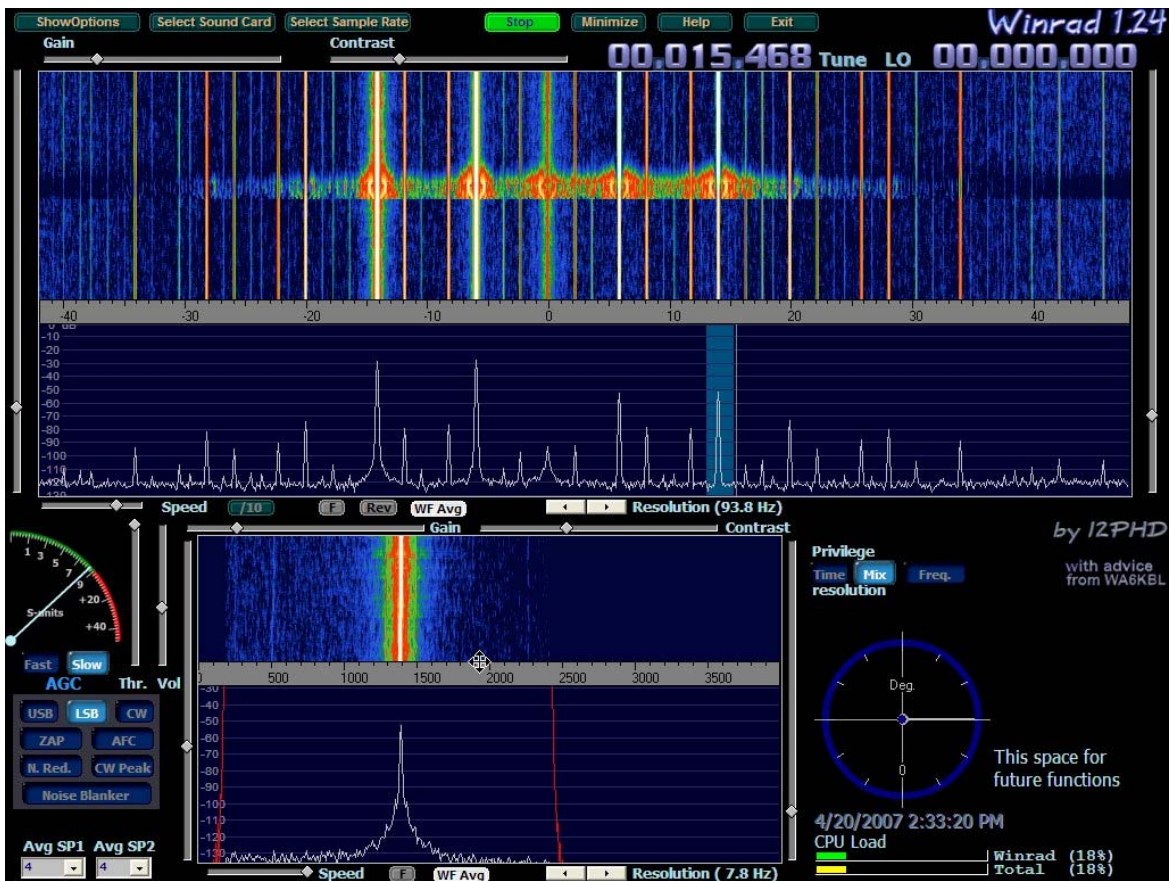7MHz Two Tones after manual hardware adjustment




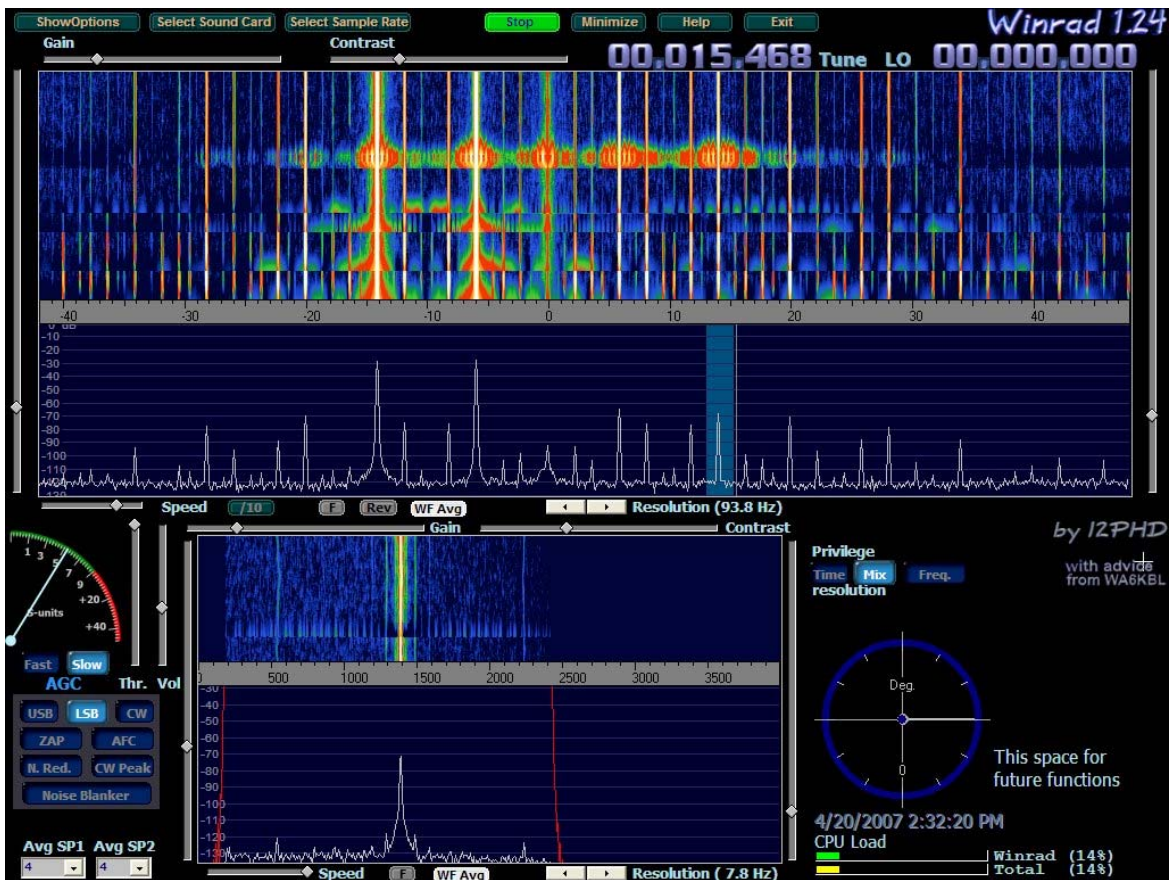28MHz Two Tones before manual hardware adjustment @ -10dBm




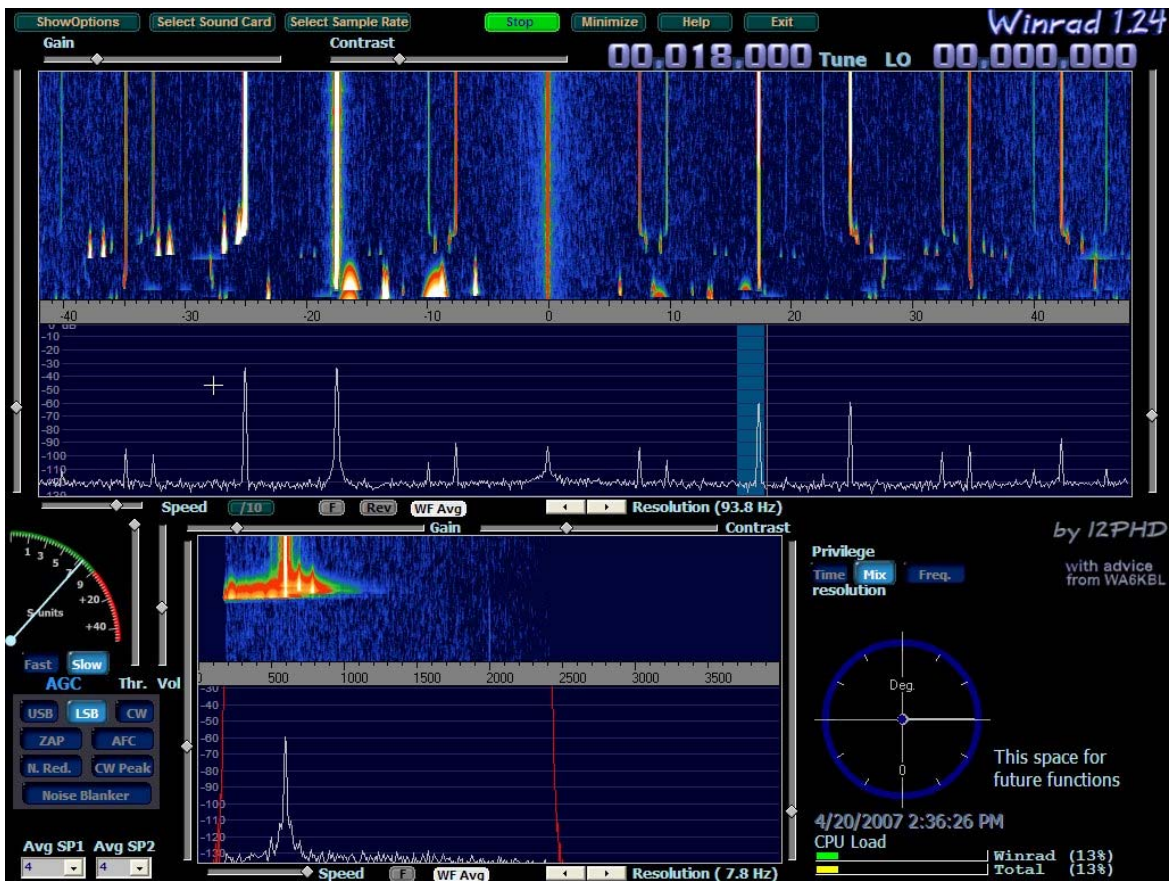28MHz Two Tones after manual hardware adjustment







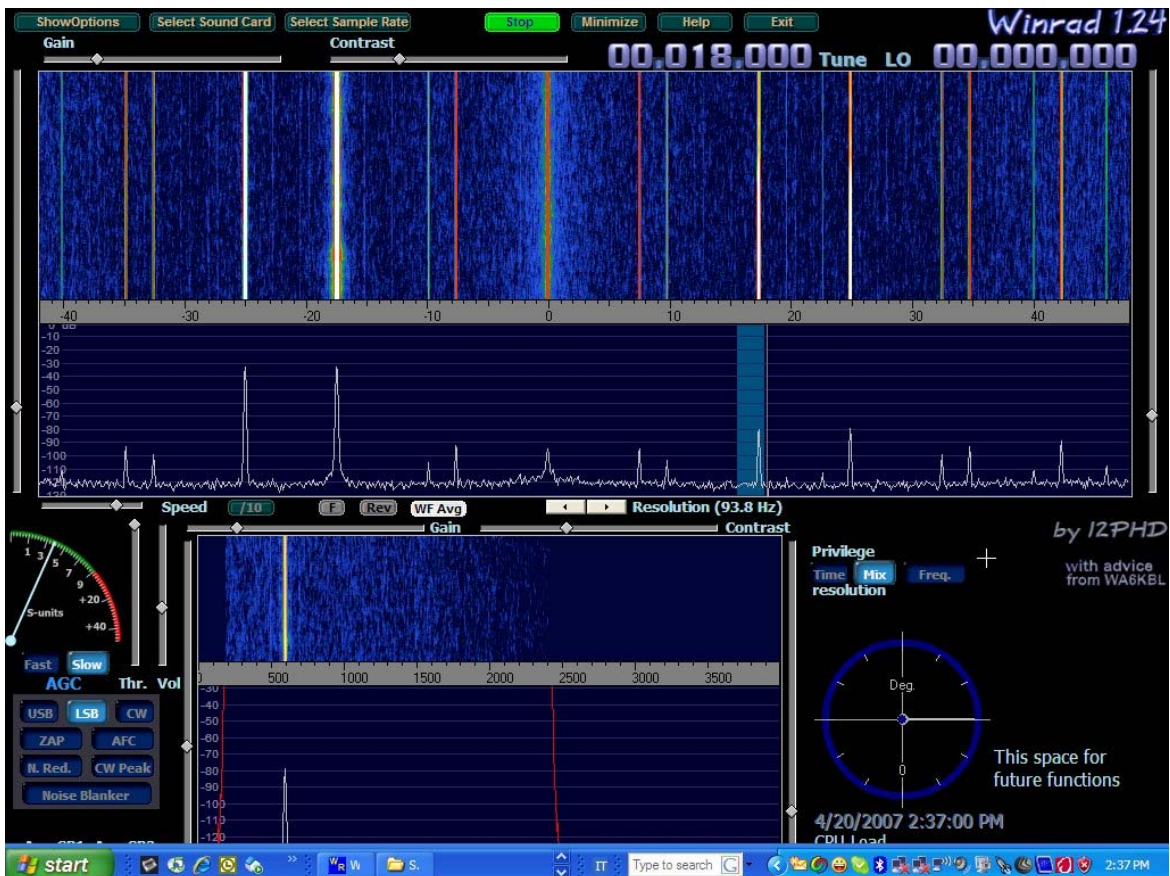
14MHz Two Tones before manual hardware adjustment @ -10dBm





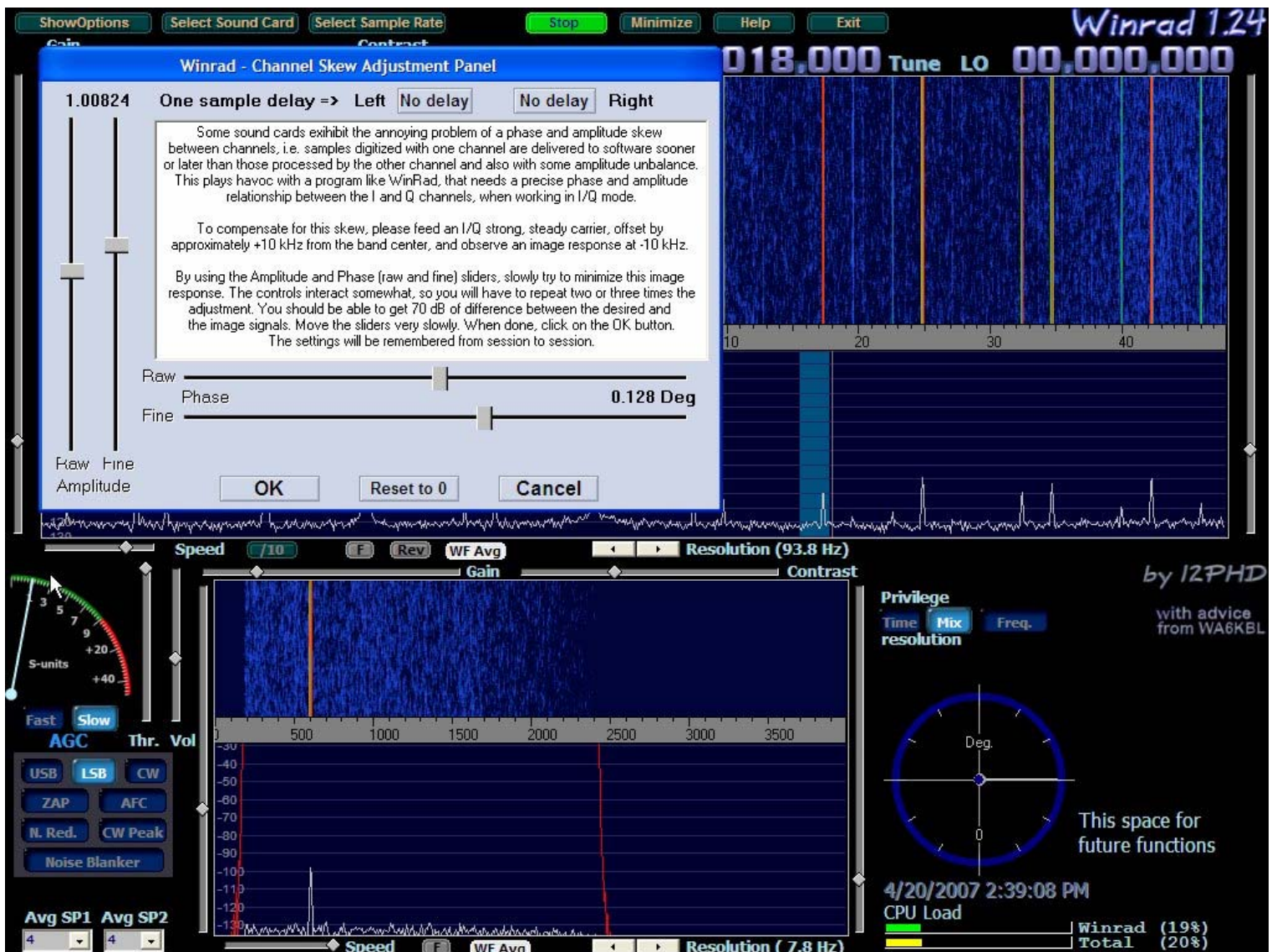14MHz Two Tones after manual hardware adjustment @ -10dBm with a total image attenuation of ca 50dB



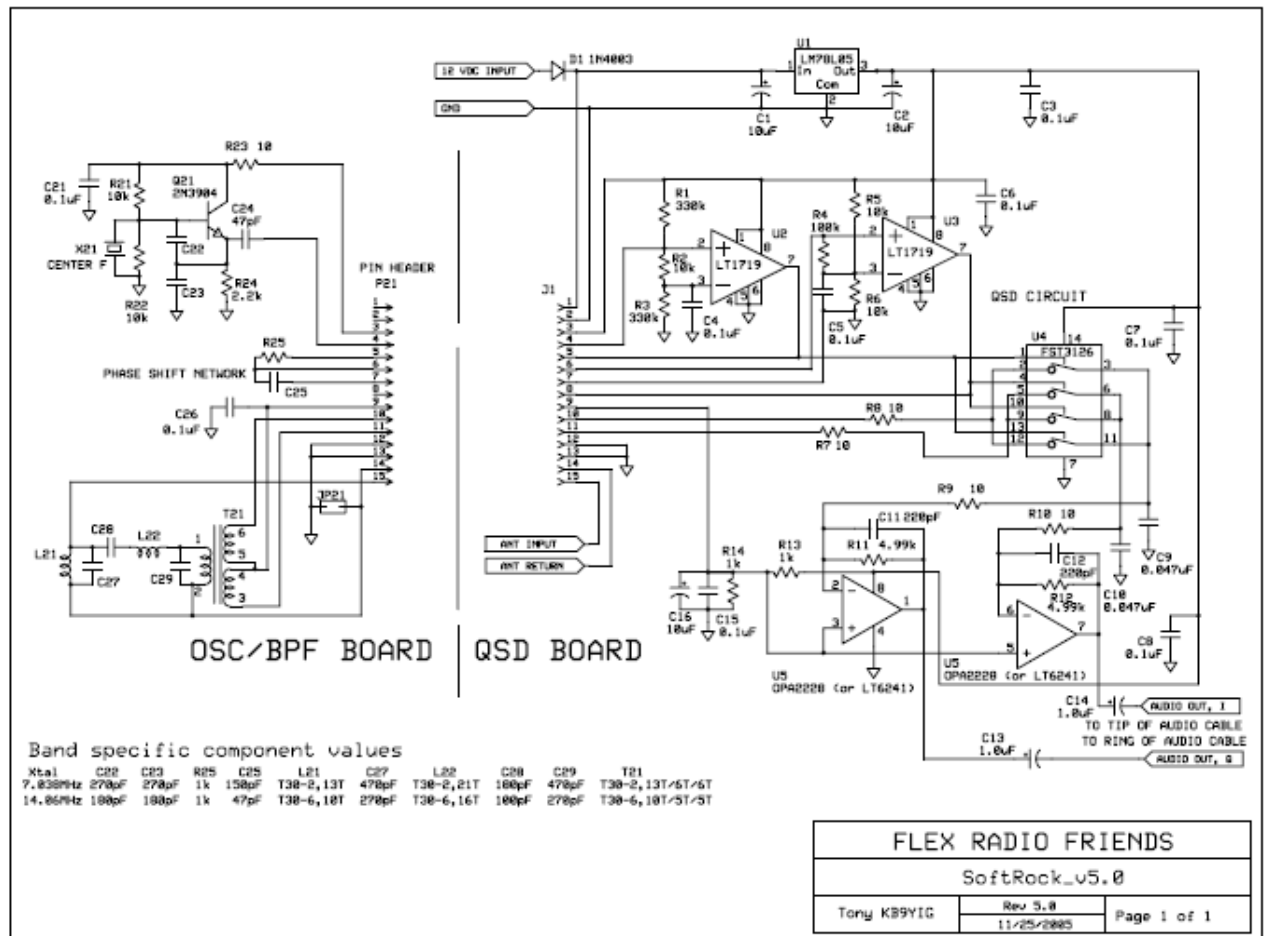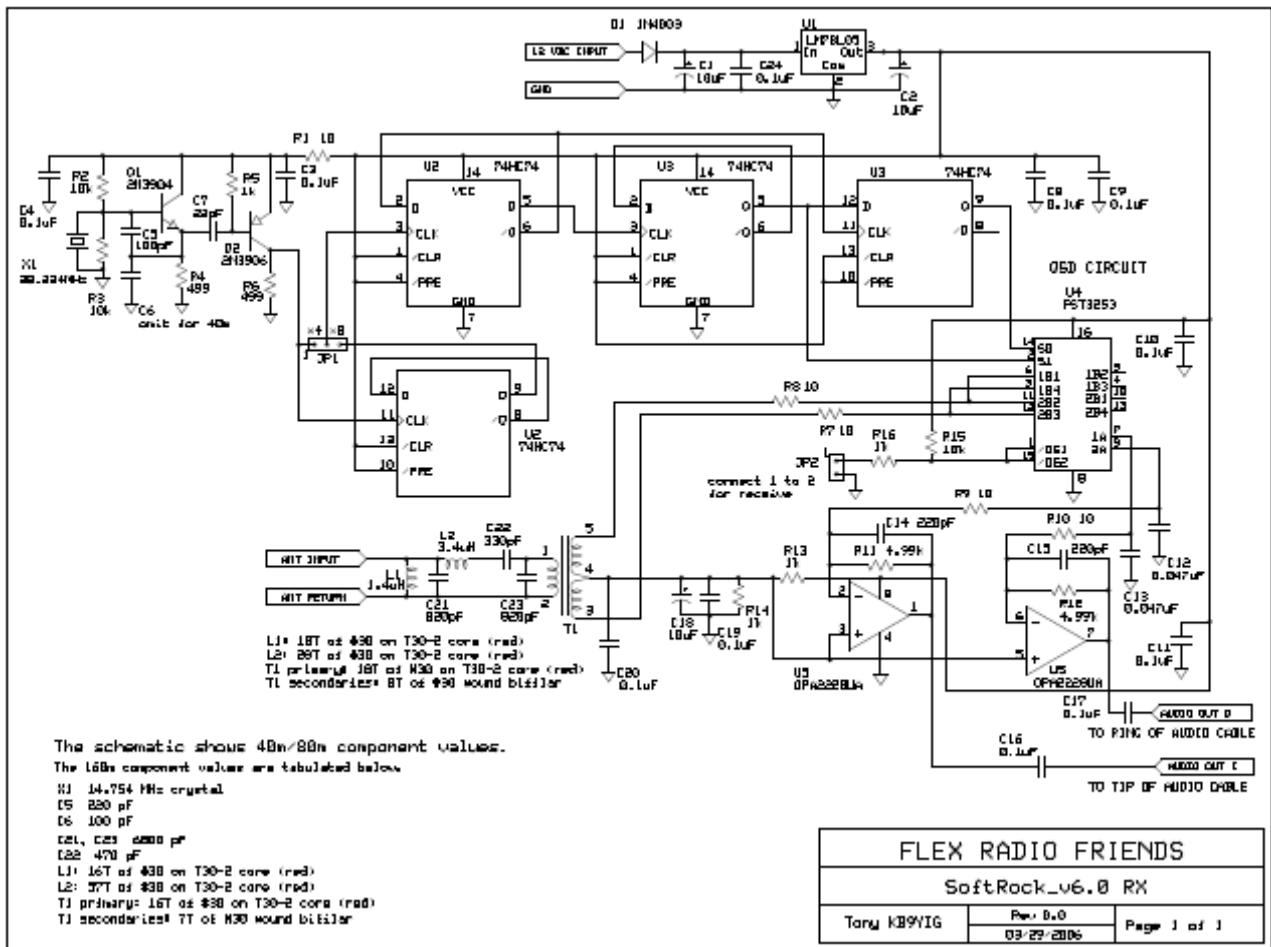14MHz Two Tones after manual hardware adjustment and Winrad software adjustment @ -10dBm  
 Here we have a total image reject attenuation of circa 70dB



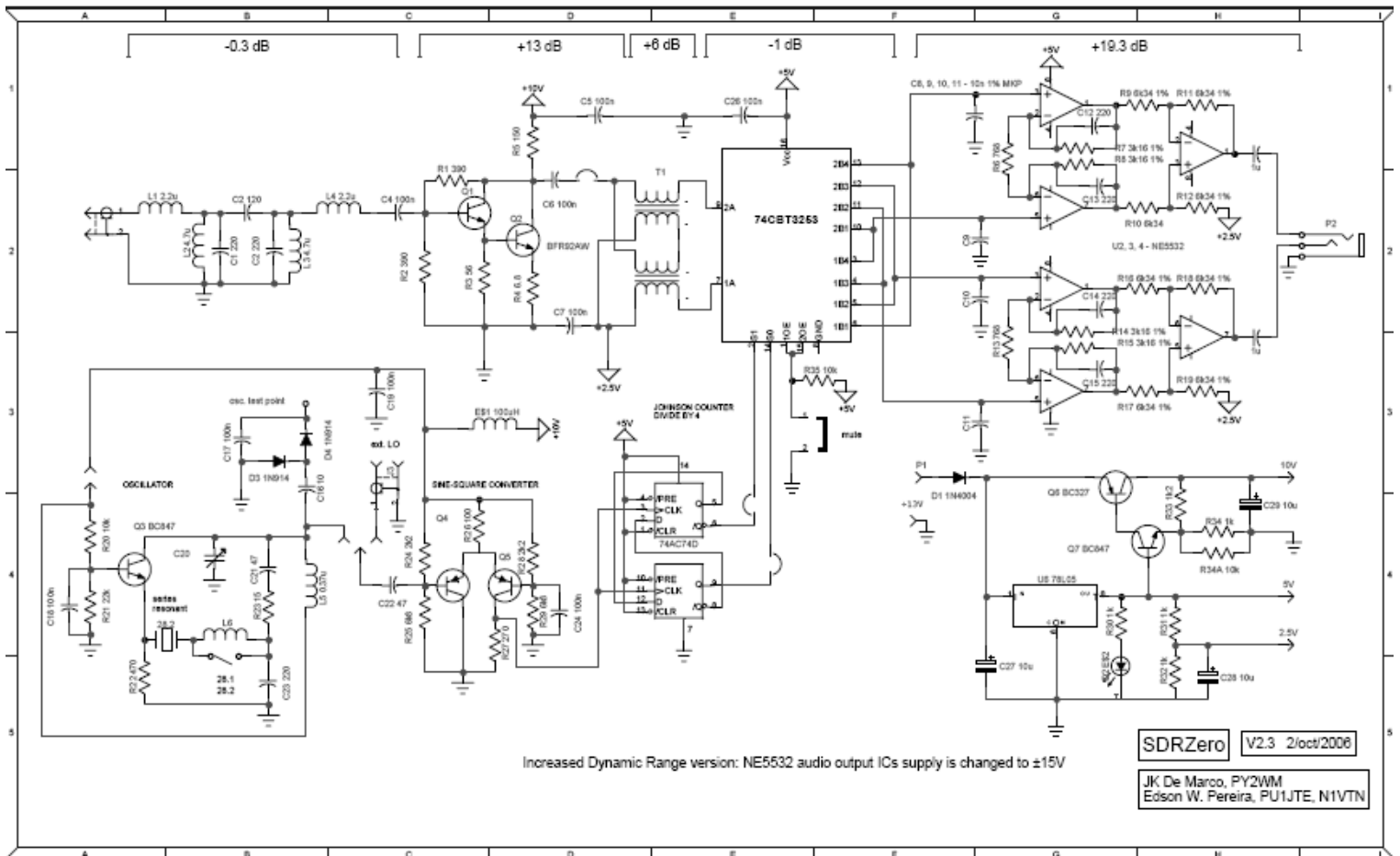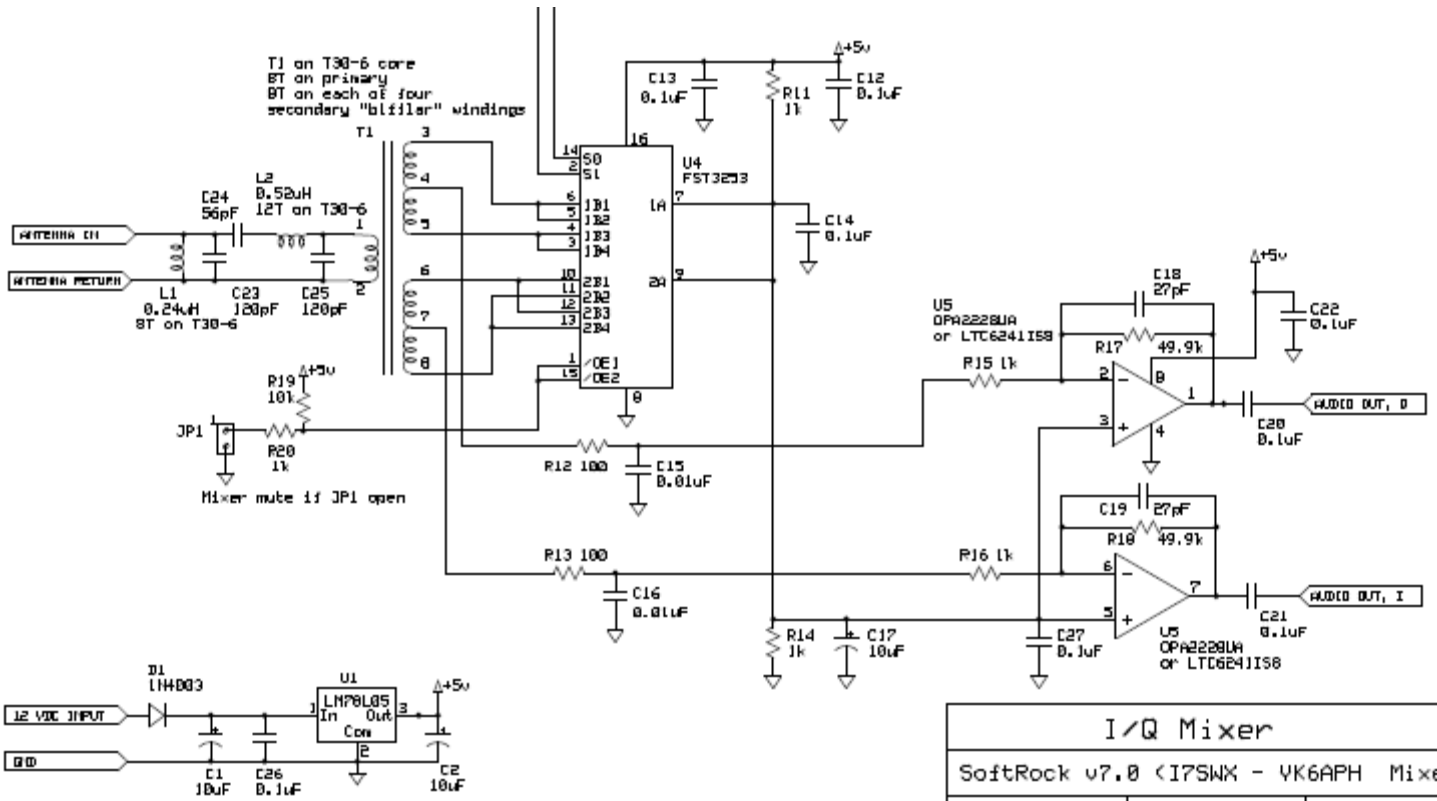

# Detector/ AF pre-amp

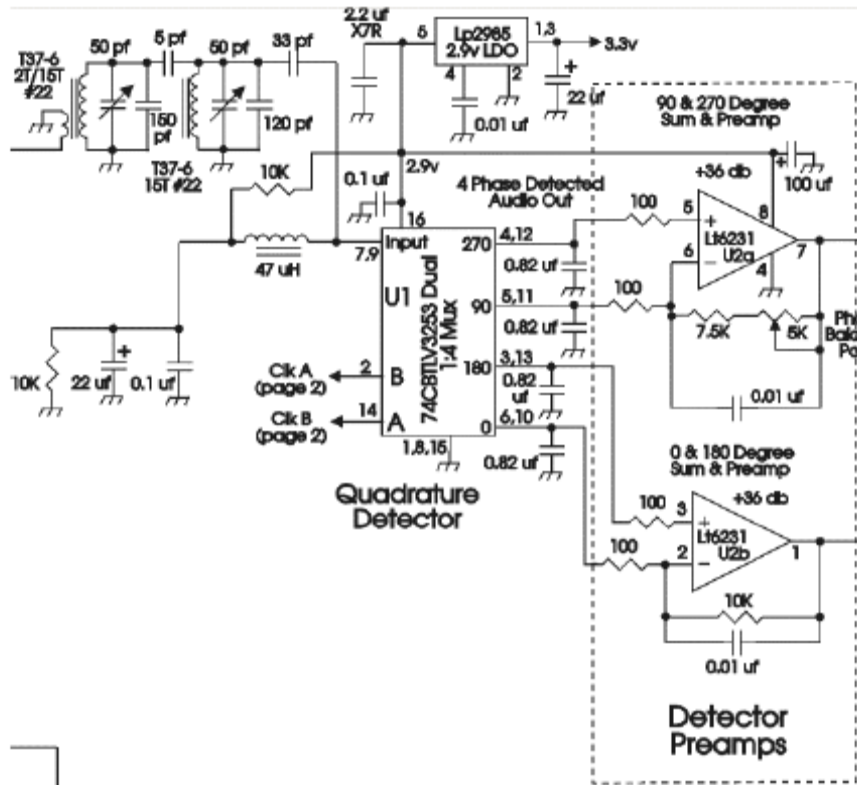


Figure 130. Tayloe quadrature detector and I/O audio preamplifier schematic

